


Homework 1

Kshitij Lakhani
EEC 281

Answer 1

OUTPUTS

| | | | |
|--------------|-----------|-----------|----------------------|
| 10a = 10000 | b = 10000 | c = 10111 | addition = 001101000 |
| 60a = 11010 | b = 10100 | c = 00111 | addition = 000000010 |
| 110a = 10101 | b = 10001 | c = 10011 | addition = 001010001 |
| 160a = 11110 | b = 11100 | c = 00011 | addition = 000000110 |
| 210a = 00000 | b = 00000 | c = 00000 | addition = 000000000 |
| 260a = 00111 | b = 00111 | c = 00111 | addition = 001011011 |
| 310a = 10000 | b = 01000 | c = 11011 | addition = 011101000 |
| 360a = 01111 | b = 11100 | c = 00111 | addition = 000110111 |
| 410a = 01100 | b = 01100 | c = 10111 | addition = 011110100 |
| 460a = 01111 | b = 00101 | c = 01001 | addition = 001101011 |
| 510a = 10101 | b = 10101 | c = 00010 | addition = 111011001 |
| 560a = 00001 | b = 00001 | c = 00001 | addition = 000001101 |
| 610a = 00100 | b = 00100 | c = 01100 | addition = 001110100 |
| 660a = 00011 | b = 00011 | c = 00011 | addition = 000100111 |
| 710a = 10110 | b = 00001 | c = 00101 | addition = 000100010 |
| 760a = 01111 | b = 10100 | c = 10011 | addition = 001110111 |

 

- All test cases – correct output

Hardware Verilog Code

```
module Top (
input [4:0] a,
input [4:0] b,
input [4:0] c,
output [8:0] addition
);
wire [8:0] sum;
wire [7:0] cout;
carrysave_3is2stage instantiated (a[4:0],b[4:0],c[4:0],sum[8:0],cout[7:0]);
assign addition[8:0] = sum[8:0] + ({cout[7:0],1'b0});
endmodule
```

```
module carriesave_3is2stage (
input [4:0] inp1,
input [4:0] inp2,
input [4:0] inp3,
output [8:0] sump,
output [7:0] coutp
);
wire [8:0] inp1_9bit;
wire [8:0] inp2_9bit;
wire [8:0] inp3_9bit;
assign inp1_9bit [8:0] = {inp1[4],inp1[4],inp1[4],inp1[4],inp1[4:0]};
assign inp2_9bit [8:0] = {inp2[4],inp2[4],inp2[4:0],1'b0,1'b0};
assign inp3_9bit [8:0] = {1'b0,inp3[4:0],1'b0,1'b0,1'b0};
FullAdder FA0 (inp1_9bit[0],inp2_9bit[0],inp3_9bit[0],sump[0],coutp[0]);
FullAdder FA1 (inp1_9bit[1],inp2_9bit[1],inp3_9bit[1],sump[1],coutp[1]);
FullAdder FA2 (inp1_9bit[2],inp2_9bit[2],inp3_9bit[2],sump[2],coutp[2]);
FullAdder FA3 (inp1_9bit[3],inp2_9bit[3],inp3_9bit[3],sump[3],coutp[3]);
FullAdder FA4 (inp1_9bit[4],inp2_9bit[4],inp3_9bit[4],sump[4],coutp[4]);
FullAdder FA5 (inp1_9bit[5],inp2_9bit[5],inp3_9bit[5],sump[5],coutp[5]);
FullAdder FA6 (inp1_9bit[6],inp2_9bit[6],inp3_9bit[6],sump[6],coutp[6]);
FullAdder FA7 (inp1_9bit[7],inp2_9bit[7],inp3_9bit[7],sump[7],coutp[7]);
FullAdder FA8 (inp1_9bit[8],inp2_9bit[8],inp3_9bit[8],sump[8], );
endmodule
```

```
module FullAdder(
input in1,
input in2,
input cin,
output sum,
output cout
);
assign sum = (in1 ^ in2) ^ cin;
assign cout = (in1 & in2) | (cin & (in1 ^ in2));
endmodule
```

Test bench Verilog Code

```
module Top_tb;
reg [4:0] a;
reg [4:0] b;
reg [4:0] c;
wire [8:0] addition;

Top testbench_addition (a[4:0],b[4:0],c[4:0],addition[8:0]);

initial
begin
$monitor ($time,"a = %b \t b = %b \t c = %b \t addition = %b \n",a[4:0],b[4:0],c[4:0],addition[8:0]);
#10
a[4:0] = 10000;
b[4:0] = 10000;
c[4:0] = 01111;
#50;
a[4:0] = 10010;
b[4:0] = 10100;
c[4:0] = 11111;
#50;
a[4:0] = 10101;
b[4:0] = 10001;
c[4:0] = 01011;
#50;
a[4:0] = 10110;
b[4:0] = 11100;
c[4:0] = 11011;
#50;
a[4:0] = 00000;
b[4:0] = 00000;
c[4:0] = 00000;
#50;
a[4:0] = 11111;
b[4:0] = 11111;
c[4:0] = 11111;
#50;
a[4:0] = 10000;
b[4:0] = 1000;
c[4:0] = 10011;
#50;
a[4:0] = 00111;
b[4:0] = 11100;
c[4:0] = 11111;
#50;
a[4:0] = 01100;
b[4:0] = 01100;
c[4:0] = 01111;
#50;
a[4:0] = 00111;
b[4:0] = 00101;
c[4:0] = 01001;
```

```

#50;
a[4:0] = 10101;
b[4:0] = 10101;
c[4:0] = 11010;
#50;
a[4:0] = 00001;
b[4:0] = 00001;
c[4:0] = 00001;
#50;
a[4:0] = 00100;
b[4:0] = 00100;
c[4:0] = 01100;
#50;
a[4:0] = 11011;
b[4:0] = 11011;
c[4:0] = 11011;
#50;
a[4:0] = 01110;
b[4:0] = 00001;
c[4:0] = 00101;
#50;
a[4:0] = 00111;
b[4:0] = 10100;
c[4:0] = 01011;
#50;
end
endmodule

```

Answer 2

OUPUTS

| | | |
|----------------------|----------------|-----------------------|
| 0mantissa = 111011 | exponent = 101 | fixed = 1111111110110 |
| 50mantissa = 011001 | exponent = 101 | fixed = 0000000110010 |
| 100mantissa = 111111 | exponent = 111 | fixed = 1111111111000 |
| 150mantissa = 100011 | exponent = 101 | fixed = 1111111000110 |
| 200mantissa = 110000 | exponent = 100 | fixed = 1111111110000 |
| 250mantissa = 011011 | exponent = 100 | fixed = 0000000011011 |
| 300mantissa = 011001 | exponent = 111 | fixed = 0000011001000 |
| 350mantissa = 011011 | exponent = 110 | fixed = 0000001101100 |
| 400mantissa = 011110 | exponent = 010 | fixed = 0011110000000 |
| 450mantissa = 111111 | exponent = 011 | fixed = 1111110000000 |
| 500mantissa = 011011 | exponent = 000 | fixed = 0000110110000 |
| 550mantissa = 111100 | exponent = 001 | fixed = 1111110000000 |
| 600mantissa = 000000 | exponent = 100 | fixed = 0000000000000 |
| 650mantissa = 000001 | exponent = 100 | fixed = 0000000000001 |
| 700mantissa = 111000 | exponent = 001 | fixed = 1111100000000 |

| | | | | | | | | | | | | | | | |
|-------------------|---------|---------|---------|---------|---------|---------|---------|---------|---------|---------|---------|---------|---------|------------------|-------|
| 6'b011001 | 6'b1... | 6'b0... | 6'b1... | 6'b1... | 6'b1... | 6'b0... | 6'b0... | 6'b0... | 6'b1... | 6'b0... | 6'b1... | 6'b0... | 6'b0... | 6'b111000 | |
| 3'b111 | 3'b101 | | 3'b111 | 3'b101 | 3'b100 | | 3'b111 | 3'b110 | 3'b010 | 3'b011 | 3'b000 | 3'b001 | 3'b100 | 3'b001 | |
| 13'b0000011001000 | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b... | 13'b111100000000 | |
| 3'h7 | 3'h5 | | 3'h7 | 3'h5 | 3'h4 | | 3'h7 | 3'h6 | 3'h2 | 3'h3 | 3'h0 | 3'h1 | 3'h4 | 3'h1 | |
| 6'h19 | 6'h3b | 6'h19 | 6'h3f | 6'h23 | 6'h30 | 6'h1b | 6'h19 | 6'h1b | 6'h1e | 6'h3f | 6'h1b | 6'h3c | 6'h00 | 6'h01 | 6'h38 |
| 13'h00c8 | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h... | 13'h1f00 | |
| | | | | | | | | | | | | | | | |

- All test cases correct output

Hardware Verilog Code

```

module float2fixed(
    mantissa,
    exponent,
    fixed);

input [2:0] exponent;
input [5:0] mantissa;
output [12:0] fixed;

wire [5:0] mantissa;
wire [2:0] exponent;
reg [12:0] fixed;

always @(*) begin
    case({exponent})

        3'b000: begin
            fixed = {mantissa[5],mantissa[5],mantissa[5],mantissa,1'b0,1'b0,1'b0,1'b0};
        end

        3'b001: begin
            fixed = {mantissa[5],mantissa[5],mantissa,1'b0,1'b0,1'b0,1'b0,1'b0};
        end

        3'b010: begin
            fixed = {mantissa[5],mantissa,1'b0,1'b0,1'b0,1'b0,1'b0,1'b0};
        end

        3'b011: begin
            fixed = {mantissa,1'b0,1'b0,1'b0,1'b0,1'b0,1'b0,1'b0};
        end

        3'b100: begin
            fixed = {mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5], mantissa};
        end
    endcase
end

```

```

3'b101: begin
fixed = {mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa,1'b0};
end

3'b110: begin
fixed = {mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa,1'b0,1'b0};
end

3'b111: begin
fixed = {mantissa[5],mantissa[5],mantissa[5],mantissa[5],mantissa,1'b0,1'b0,1'b0};
end
endcase
end
endmodule

```

Test bench Verilog Code

```

module float2fixed_tb;
reg [5:0] mantissa;
reg [2:0] exponent;
wire [12:0] fixed;

float2fixed FF(mantissa[5:0],exponent[2:0], fixed[12:0]);

initial
begin

$monitor($time, "mantissa = %b \t exponent = %b \t fixed = %b \t",mantissa[5:0],exponent[2:0],fixed[12:0]);

mantissa[5:0] = 6'b111011;
exponent[2:0] = 3'b101;
#50;

mantissa[5:0] = 6'b011001;
exponent[2:0] = 3'b101;
#50;

mantissa[5:0] = 6'b111111;
exponent[2:0] = 3'b111;
#50;

mantissa[5:0] = 6'b100011;
exponent[2:0] = 3'b101;
#50;

mantissa[5:0] = 6'b110000;
exponent[2:0] = 3'b100;
#50;

mantissa[5:0] = 6'b011011;
exponent[2:0] = 3'b100;
#50;

```

[illegible]

| | | | |
|-----|-----------------------------|-----------------|----------------|
| 0 | Fixed Point Input = xxxxxxx | Mantissa = xxxx | Exponent = xxx |
| 10 | Fixed Point Input = 1000100 | Mantissa = 1000 | Exponent = 000 |
| 60 | Fixed Point Input = 1011010 | Mantissa = 1011 | Exponent = 000 |
| 110 | Fixed Point Input = 1011100 | Mantissa = 1011 | Exponent = 000 |
| 160 | Fixed Point Input = 0000100 | Mantissa = 0100 | Exponent = 101 |
| 210 | Fixed Point Input = 1110010 | Mantissa = 1001 | Exponent = 110 |
| 260 | Fixed Point Input = 0100110 | Mantissa = 0100 | Exponent = 000 |
| 310 | Fixed Point Input = 1111000 | Mantissa = 1000 | Exponent = 101 |
| 360 | Fixed Point Input = 1110000 | Mantissa = 1000 | Exponent = 110 |
| 410 | Fixed Point Input = 0110100 | Mantissa = 0110 | Exponent = 000 |
| 460 | Fixed Point Input = 1000110 | Mantissa = 1000 | Exponent = 000 |
| 510 | Fixed Point Input = 0010000 | Mantissa = 0100 | Exponent = 111 |
| 560 | Fixed Point Input = 1100100 | Mantissa = 1001 | Exponent = 111 |
| 610 | Fixed Point Input = 0011010 | Mantissa = 0110 | Exponent = 111 |
| 660 | Fixed Point Input = 1000110 | Mantissa = 1000 | Exponent = 000 |
| 710 | Fixed Point Input = 1101000 | Mantissa = 1010 | Exponent = 111 |

- All test cases correct output

Hardware + Test bench Verilog Code

```

module fixedtofloating;
reg [6:0] fixed;
reg [3:0] mantissa;
reg [2:0] exponent;
always @ (*) begin
if (fixed[5] != fixed[6]) begin
mantissa[3:0] = {fixed[6],fixed[5],fixed[4],fixed[3]};
exponent[2:0] = 3'b000;
end else if (fixed[4] != fixed[6]) begin
mantissa[3:0] = {fixed[5],fixed[4],fixed[3],fixed[2]};
exponent[2:0] = 3'b111;
end else if (fixed[3] != fixed[6]) begin
mantissa[3:0] = {fixed[4],fixed[3],fixed[2],fixed[1]};
exponent[2:0] = 3'b110;
end else if (fixed[2] != fixed[6]) begin
mantissa[3:0] = {fixed[3],fixed[2],fixed[1],fixed[0]};
exponent[2:0] = 3'b101;
end else begin
mantissa[3:0] = {fixed[2],fixed[1],fixed[0],1'b0};
exponent[2:0] = 3'b100;
end
end
end

```



```

initial
begin
$monitor($time," Fixed Point Input = %b \t Mantissa = %b \t Exponent = %b \n",fixed[6:0],mantissa[3:0],exponent[2:0]);
#10;
fixed[6:0] = 1100100;
#50;
fixed[6:0] = 1010010;
#50;
fixed[6:0] = 0011100;
#50;
fixed[6:0] = 0100100;
#50;
fixed[6:0] = 0001010;
#50;
fixed[6:0] = 1011110;
#50;
fixed[6:0] = 0011000;
#50;
fixed[6:0] = 1110000;
#50;
fixed[6:0] = 1010100;
#50;
fixed[6:0] = 1111110;
#50;
fixed[6:0] = 0010000;
#50;
fixed[6:0] = 0000100;
#50;
fixed[6:0] = 0010010;
#50;
fixed[6:0] = 1111110;
#50;
fixed[6:0] = 0001000;
#50;
end
endmodule

```

Answer 4


| inputs | | | | | | outputs | | |
|--------|---|---|---|---|---|---------|---|-----|
| | | | | | | c | | c c |
| a | b | c | d | i | | o | 1 | s |
| ----- | | | | | + | ----- | | |
| 0 | 0 | 0 | 0 | 0 | | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | | 0 | 1 | 0 |

| | | | | | | | | |
|---|---|---|---|---|--|---|---|---|
| 0 | 1 | 0 | 1 | 1 | | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 1 | | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 0 | | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 | | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 0 | | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | | 1 | 1 | 1 |

Answer 5

OUTPUTS

| | | | | |
|-----|----------------|---------|---------|----------|
| 0 | input is xxxxx | c0 is x | c1 is x | sum is x |
| 50 | input is 11110 | c0 is 1 | c1 is 1 | sum is 0 |
| 100 | input is 00000 | c0 is 0 | c1 is 0 | sum is 0 |
| 150 | input is 10001 | c0 is 0 | c1 is 1 | sum is 0 |
| 200 | input is 00101 | c0 is 1 | c1 is 0 | sum is 0 |

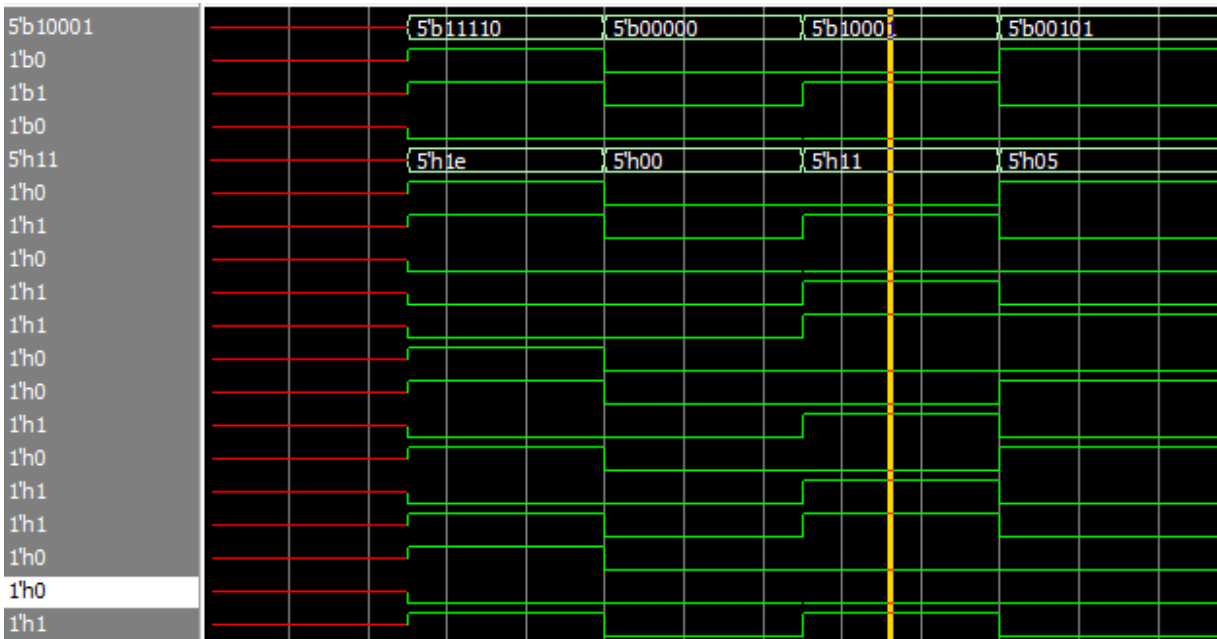

- All test cases correct output

Hardware Verilog Code

```
module carrysave_4is2 (
input [4:0] in,
output c0,
output c1,
output sum
);
wire connection;
FullAdder FA0 (in[0],in[1],in[2],connection,c0);
FullAdder FA1 (connection,in[4],in[3],sum,c1);
endmodule
```

```
module FullAdder(
input in1,
input in2,
input cin,
output sum,
output cout
);
assign sum = (in1 ^ in2) ^ cin;
assign cout = (in1 & in2) | (cin & (in1 ^ in2));
endmodule
```

Test bench Verilog Code

```
module carrysave_4is2_tb;
reg [4:0] in;
wire c0,c1,sum;
carrysave_4is2 carrysave_tb(in[4:0],c0,c1,sum);
initial
begin
$monitor($time,"input is %b \t c0 is %b \t c1 is %b \t sum is %b \n",in[4:0],c0,c1,sum);
#50;
in[4:0] = 10110;
#50
in[4:0] = 00000;
#50;
in[4:0] = 10001;
#50;
in[4:0] = 00101;
end
endmodule
```

Answer 6

OUTPUTS

| inp1 | inp2 | inp3 | inp4 | inp5 | inp6 | answerp |
|-----------------|-------------|-------------|-------------|-------------|-------------|------------------|
| 0inp1 = xxxx | inp2 = xxxx | inp3 = xxxx | inp4 = xxxx | inp5 = xxxx | inp6 = xxxx | answerp = xxxxxx |
| 5inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000000 |
| 55inp1 = 0001 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000001 |
| 105inp1 = 0000 | inp2 = 0001 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000001 |
| 155inp1 = 0000 | inp2 = 0000 | inp3 = 0001 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000001 |
| 205inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0001 | inp5 = 0000 | inp6 = 0000 | answerp = 000001 |
| 255inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0001 | inp6 = 0000 | answerp = 000001 |
| 305inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0001 | answerp = 000001 |
| 355inp1 = 1111 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111111 |
| 405inp1 = 0000 | inp2 = 1111 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111111 |
| 455inp1 = 0000 | inp2 = 0000 | inp3 = 1111 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111111 |
| 505inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 1111 | inp5 = 0000 | inp6 = 0000 | answerp = 111111 |
| 555inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 1111 | inp6 = 0000 | answerp = 111111 |
| 605inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 1111 | answerp = 111111 |
| 655inp1 = 0111 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000111 |
| 705inp1 = 0000 | inp2 = 0111 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000111 |
| 755inp1 = 0000 | inp2 = 0000 | inp3 = 0111 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000111 |
| 805inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0111 | inp5 = 0000 | inp6 = 0000 | answerp = 000111 |
| 855inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0111 | inp6 = 0000 | answerp = 000111 |
| 905inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0111 | answerp = 000111 |
| 955inp1 = 1000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111000 |
| 1005inp1 = 0000 | inp2 = 1000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111000 |
| 1055inp1 = 0000 | inp2 = 0000 | inp3 = 1000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 111000 |
| 1105inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 1000 | inp5 = 0000 | inp6 = 0000 | answerp = 111000 |
| 1155inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 1000 | inp6 = 0000 | answerp = 111000 |
| 1205inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 1000 | answerp = 111000 |
| 1255inp1 = 0001 | inp2 = 0001 | inp3 = 0001 | inp4 = 0001 | inp5 = 0001 | inp6 = 0001 | answerp = 001010 |
| 1305inp1 = 1111 | inp2 = 1111 | inp3 = 1111 | inp4 = 1111 | inp5 = 1111 | inp6 = 1111 | answerp = 110110 |
| 1355inp1 = 0001 | inp2 = 0010 | inp3 = 0011 | inp4 = 0100 | inp5 = 0101 | inp6 = 0110 | answerp = 100011 |
| 1405inp1 = 0110 | inp2 = 0101 | inp3 = 0101 | inp4 = 0101 | inp5 = 0101 | inp6 = 0101 | answerp = 110011 |
| 1455inp1 = 0000 | inp2 = 0000 | inp3 = 0000 | inp4 = 0000 | inp5 = 0000 | inp6 = 0000 | answerp = 000000 |
| 1505inp1 = 1001 | inp2 = 1011 | inp3 = 1011 | inp4 = 1011 | inp5 = 1011 | inp6 = 1011 | answerp = 001100 |

- All test cases, except last 5 – correct/expected output

Hardware Verilog Code

```

module stage1_3is2 (
input [5:0] in1,
input [5:0] in2,
input [5:0] in3,
output [5:0] cout_stage1,
output [5:0] sum_stage1
);
FullAdder FA2 (in1[0],in2[0],in3[0],sum_stage1[0],cout_stage1[0]);
FullAdder FA3 (in1[1],in2[1],in3[1],sum_stage1[1],cout_stage1[1]);
FullAdder FA4 (in1[2],in2[2],in3[2],sum_stage1[2],cout_stage1[2]);
FullAdder FA5 (in1[3],in2[3],in3[3],sum_stage1[3],cout_stage1[3]);
FullAdder FA12 (in1[4],in2[4],in3[4],sum_stage1[4],cout_stage1[4]);
FullAdder FA13 (in1[5],in2[5],in3[5],sum_stage1[5],cout_stage1[5]);
endmodule

```

```

module stage2_3is2 (
input [5:0] in4,
input [5:0] in5,
input [5:0] in6,
output [5:0] cout_stage2,
output [5:0] sum_stage2
);
FullAdder FA6 (in4[0],in5[0],in6[0],sum_stage2[0],cout_stage2[0]);
FullAdder FA7 (in4[1],in5[1],in6[1],sum_stage2[1],cout_stage2[1]);
FullAdder FA8 (in4[2],in5[2],in6[2],sum_stage2[2],cout_stage2[2]);
FullAdder FA9 (in4[3],in5[3],in6[3],sum_stage2[3],cout_stage2[3]);
FullAdder FA22 (in4[4],in5[4],in6[4],sum_stage2[4],cout_stage2[4]);
FullAdder FA23 (in4[5],in5[5],in6[5],sum_stage2[5],cout_stage2[5]);

```

```
endmodule
```

```
module stage3_4is2 (  
input [5:0] subin1,  
input [5:0] subin2,  
input [5:0] subin3,  
input [5:0] subin4,  
output [5:0] sum_stage3,  
output [5:0] cout_stage3  
//output carry  
);  
wire connection1,connection2,connection3,connection4,connection5;  
carrysav_4is2 CS1(({1'b0,1'b0,subin3[0],1'b0,subin1[0]}),connection1,cout_stage3[0],sum_stage3[0]);  
carrysav_4is2 CS2(({connection1,subin4[0],subin3[1],subin2[0],subin1[1]}),connection2,cout_stage3[1],sum_stage3[1]);  
carrysav_4is2 CS3(({connection2,subin4[1],subin3[2],subin2[1],subin1[2]}),connection3,cout_stage3[2],sum_stage3[2]);  
carrysav_4is2 CS4(({connection3,subin4[2],subin3[3],subin2[2],subin1[3]}),connection4,cout_stage3[3],sum_stage3[3]);  
carrysav_4is2 CS5(({connection4,subin4[3],subin3[4],subin2[3],subin1[4]}),connection5,cout_stage3[4],sum_stage3[4]);  
carrysav_4is2 CS6(({connection5,subin4[4],subin3[5],subin2[4],subin1[5]}),, ,sum_stage3[5]);  
endmodule
```

```
module Top (  
input [3:0] i1,  
input [3:0] i2,  
input [3:0] i3,  
input [3:0] i4,  
input [3:0] i5,  
input [3:0] i6,  
output [5:0] answer  
);  
wire [5:0] cout_S1;  
wire [5:0] sum_S1;  
wire [5:0] cout_S2;  
wire [5:0] sum_S2;  
wire [5:0] sum_S3;  
wire [5:0] cout_S3;  
//wire carry_S3;  
stage1_3is2 S1 ( { i1[3],i1[3],i1[3:0]} , {i2[3],i2[3],i2[3:0]} , {i3[3],i3[3],i3[3:0]} , cout_S1[5:0] , sum_S1[5:0]);  
stage2_3is2 S2 ( {i4[3],i4[3],i4[3:0]} , {i5[3],i5[3],i5[3:0]} , {i6[3],i6[3],i6[3:0]} , cout_S2[5:0] , sum_S2[5:0]);  
stage3_4is2 S3 (sum_S1[5:0],({cout_S1[4:0],1'b0}),sum_S2[5:0],({cout_S2[4:0],1'b0}),sum_S3[5:0],cout_S3[5:0]/*,carry_S3*/);  
assign answer [5:0] = (sum_S3[5:0]) + ({cout_S3[4:0],1'b0});  
endmodule
```

```
module carriesav_4is2 (  
input [4:0] in,  
output c0,  
output c1,  
output sum  
);  
wire connection;  
FullAdder FA0 (in[0],in[1],in[2],connection,c0);  
FullAdder FA1 (connection,in[4],in[3],sum,c1);  
endmodule
```

```
module FullAdder(  
input [3:0] i1,  
input [3:0] i2,  
input [3:0] i3,  
output [5:0] sum,  
output [5:0] cout
```

```

input in1,
input in2,
input cin,
output sum,
output cout
);
assign sum = (in1 ^ in2) ^ cin;
assign cout = (in1 & in2) | (cin & (in1 ^ in2));
endmodule

```

Test bench Verilog Code

```

module Top_tb;
reg [3:0] inp1;
reg [3:0] inp2;
reg [3:0] inp3;
reg [3:0] inp4;
reg [3:0] inp5;
reg [3:0] inp6;
wire [5:0] answerp;
TopToptestbench (inp1 [3:0],inp2 [3:0],inp3 [3:0],inp4 [3:0],inp5 [3:0],inp6 [3:0],answerp [5:0]);

initial
begin
$monitor ($time, "inp1 = %b \t inp2 = %b \t inp3 = %b \t inp4 = %b \t inp5 = %b \t inp6 = %b \t answerp = %b \t",inp1[3:0],inp2[3:0],inp3[3:0],inp4[3:0],inp5[3:0],inp6[3:0],answerp[5:0]);
#5;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0001;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0001;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0001;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;

```

```
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0001;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0001;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0001;
#50;
inp1[3:0] = 4'b1111;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b1111;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b1111;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b1111;
inp4[3:0] = 4'b1111;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
```

```
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b1111;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b1111;
#50;
inp1[3:0] = 4'b0111; //7
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0111;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0111;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0111;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0111;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0111;
#50;
inp1[3:0] = 4'b1000;
```



```
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b1000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b1000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b1000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b1000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b1000;
#50;
inp1[3:0] = 4'b0001;
inp2[3:0] = 4'b0001;
inp3[3:0] = 4'b0001;
inp4[3:0] = 4'b0001;
inp5[3:0] = 4'b0001;
inp6[3:0] = 4'b0001;
#50;
inp1[3:0] = 4'b1111;
inp2[3:0] = 4'b1111;
inp3[3:0] = 4'b1111;
inp4[3:0] = 4'b1111;
inp5[3:0] = 4'b1111;
inp6[3:0] = 4'b1111;
```

```

#50;
inp1[3:0] = 4'b0001;
inp2[3:0] = 4'b0010;
inp3[3:0] = 4'b0011;
inp4[3:0] = 4'b0100;
inp5[3:0] = 4'b0101;
inp6[3:0] = 4'b0110;
#50;
inp1[3:0] = 4'b0110;
inp2[3:0] = 4'b0101;
inp3[3:0] = 4'b0101;
inp4[3:0] = 4'b0101;
inp5[3:0] = 4'b0101;
inp6[3:0] = 4'b0101;
#50;
inp1[3:0] = 4'b0000;
inp2[3:0] = 4'b0000;
inp3[3:0] = 4'b0000;
inp4[3:0] = 4'b0000;
inp5[3:0] = 4'b0000;
inp6[3:0] = 4'b0000;
#50;
inp1[3:0] = 4'b1001; //-7
inp2[3:0] = 4'b1011; //-5
inp3[3:0] = 4'b1011; //-5
inp4[3:0] = 4'b1011; //-5
inp5[3:0] = 4'b1011; //-5
inp6[3:0] = 4'b1011; //-5
#100;
end
endmodule

```

Answer 7

```

module carriesave_4is2 (
input [4:0] in,
output c0,
output c1,
output sum
);
wire connection;
FullAdder FA0 (in[0],in[1],in[2],connection,c0);
FullAdder FA1 (connection,in[4],in[3],sum,c1);
endmodule

```

```

module Top1 (
input [10:0] inp,
output cout,
output sum
);
wire [3:0] sum_word;

```

```

wire [3:0] carry_word;
wire cs1_c0;
wire cs1_c1;
wire cs1_s;
wire cs2_c0;
wire cs2_c1;
wire cs2_s;
stage1 instantiated(inp[10:0],sum_word[3:0],carry_word[3:0]);

carrysave_4is2 cs1 ({sum_word[3],carry_word[3],sum_word[2],carry_word[2]},cs1_c0,cs1_c1,cs1_s);
carrysave_4is2 cs2 ({sum_word[1],carry_word[1],sum_word[0],carry_word[0]},cs2_c0,cs2_c1,cs2_s);
carrysave_4is2 cs3 ({cs1_c1,cs1_s,cs2_c1,cs2_s},)

//assign addition[4:0] = {1'b0,sum_word[3:0]} + {carry_word[3:0],1'b0};
endmodule

module stage1 (
input [10:0] in,
output [3:0] sum,
output [3:0] cout
);

FullAdder FA0 (in[0],in[1],in[2],sum[0],cout[0]);
FullAdder FA1 (in[3],in[4],in[5],sum[1],cout[1]);
FullAdder FA2 (in[6],in[7],in[8],sum[2],cout[2]);

HalfAdder HA (in[9],in[10],sum[3],cout[3]);
endmodule

module HalfAdder(
input inp1,
input inp2,
output sum,
output cout
);
assign sum = inp1 ^ inp2;
assign cout = inp1 & inp2;
endmodule

module FullAdder(
input in1,
input in2,
input cin,
output sum,
output cout
);
assign sum = (in1 ^ in2) ^ cin;
assign cout = (in1 & in2) | (cin & (in1 ^ in2));
endmodule

```

- Works for few test cases only erratically